

The background is a solid dark blue. A central gold-outlined rectangle contains the text. Several thin, gold-colored lines radiate from the corners and sides of this rectangle, extending towards the edges of the frame. These lines are of varying lengths and angles, creating a starburst or network-like effect.

Control Unit

IF/ID

TABLE OF CONTENTS

1. IMPLEMENTATION OF CONTROL UNIT

Determining the opcodes of instructions and control signals

2. CONDITIONAL OPERATOR (NESTED)

Introducing a useful operator used for inspecting multiple conditions

3. IMPLEMENTATION OF IF/ID REGISTER

Implementing IF/ID pipeline register to store required data

4. INTEGRATING ALL MODULES

Integrate all modules which have been implemented up to now

5. INPUTS & OUTPUTS

Describe inputs and outputs of required modules

1. IMPLEMENTATION OF CONTROL UNIT

Instruction	Control Signals								
	OpCode	Reg Dst	ALU Src	Memto Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp
R-type	000000	1	0	0	1	0	0	0	000
lw	000100	0	1	1	1	1	0	0	011
sw	000101	0	1	0	0	0	1	0	011
addi	000111	0	1	0	1	0	0	0	011
beq	000110	0	0	0	0	0	0	1	001
slti	000001	0	1	0	1	0	0	0	010

2. CONDITIONAL OPERATOR (NESTED)


Just like the ternary operator in C (?:)

Example:


```
assign out = sel == 2'b00 ? a :  
            sel == 2'b01 ? b :  
            sel == 2'b01 ? c :  
            sel == 2'b01 ? d : 1'b0;
```

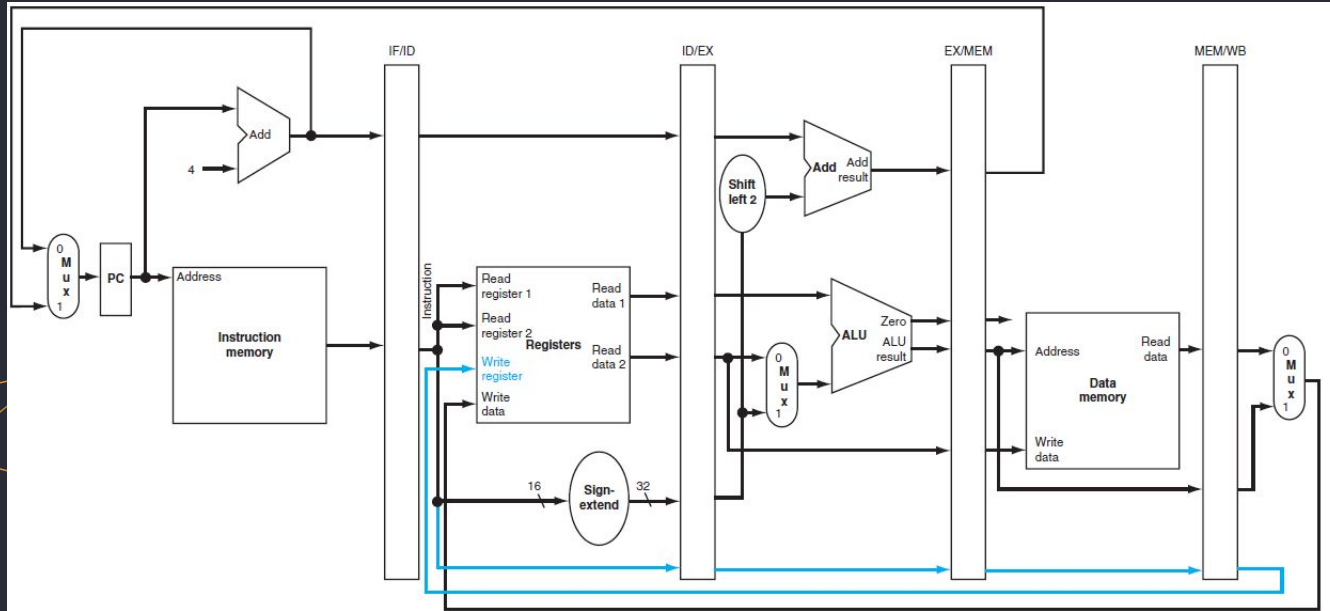3. INTRODUCTION TO PIPELINE REGISTERS

- Placed between Fetch & Decode stages
- The outputs are produced on the positive edge of the clock in the stages, therefore, to make sure the data from pipeline registers are reliable, they need to output on the negative edge of the clock



4. INTEGRATING ALL MODULES

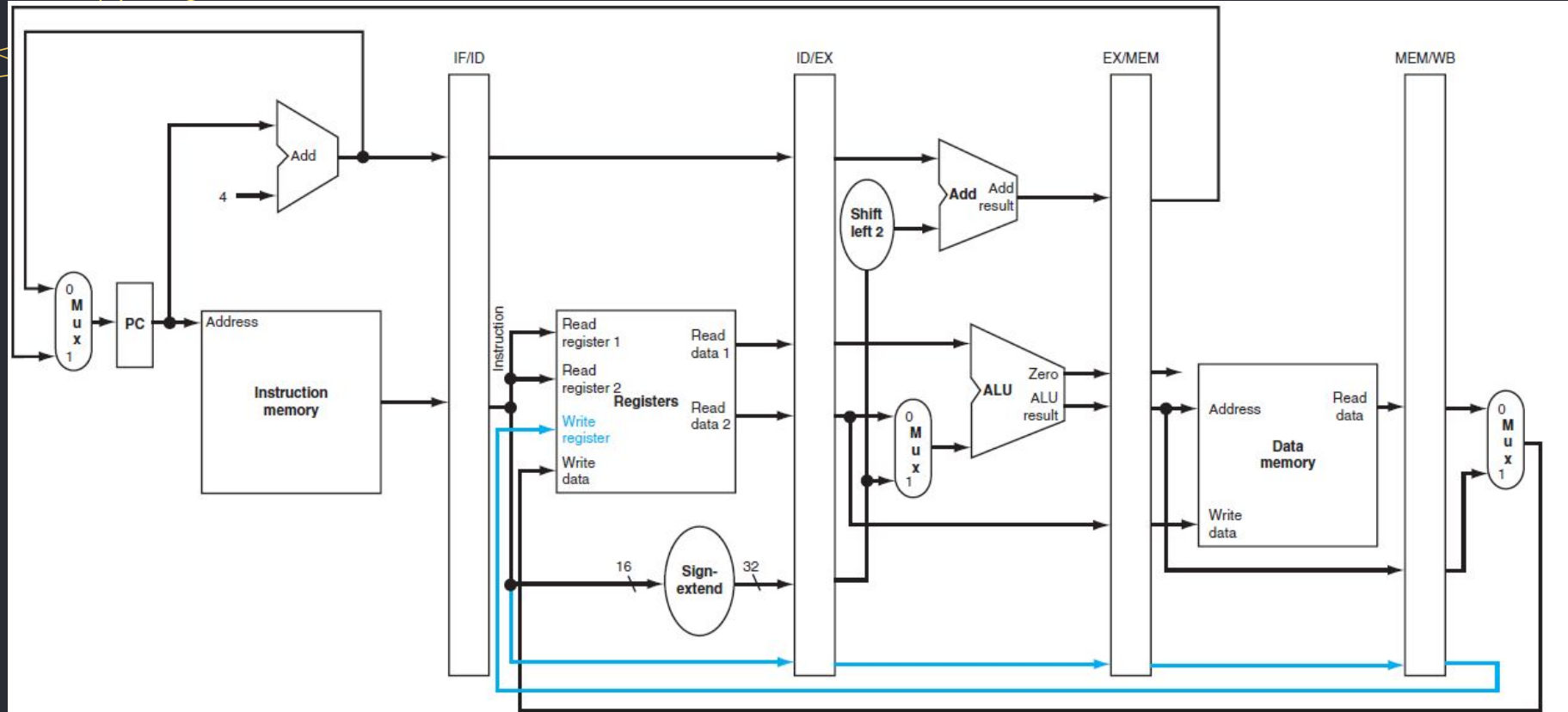

5. INPUTS & OUTPUTS

Finally, it's time to instantiate the modules and connect them together. Modules which need to be instantiated and connected are as follows:

Control Unit:

- Inputs: Opcode (6 bits)
- Outputs: RegDst (1), ALUSrc (1), MemtoReg (1), RegWrite (1), MemRead (1), MemWrite (1), Branch (1), ALUOp (2)

IF/ID Register:

- Inputs: clk(1), next_pc (32), instruction (32), hit (1)
- Outputs: instruction_out (32), next_pc_out (32), hit_out (1)

MIPS: (Instantiate Fetch, IF/ID Register, Decode, Control Unit)